
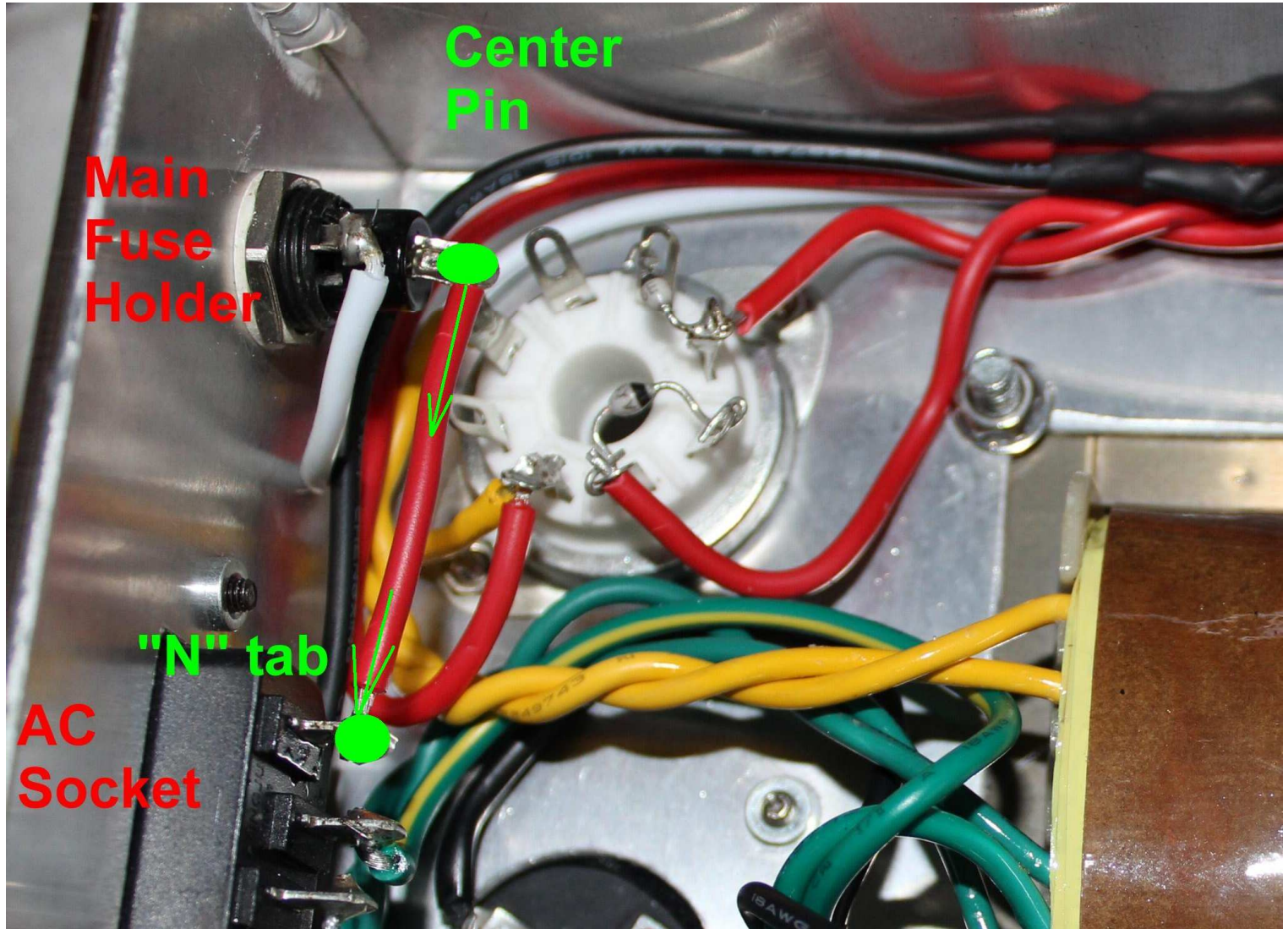


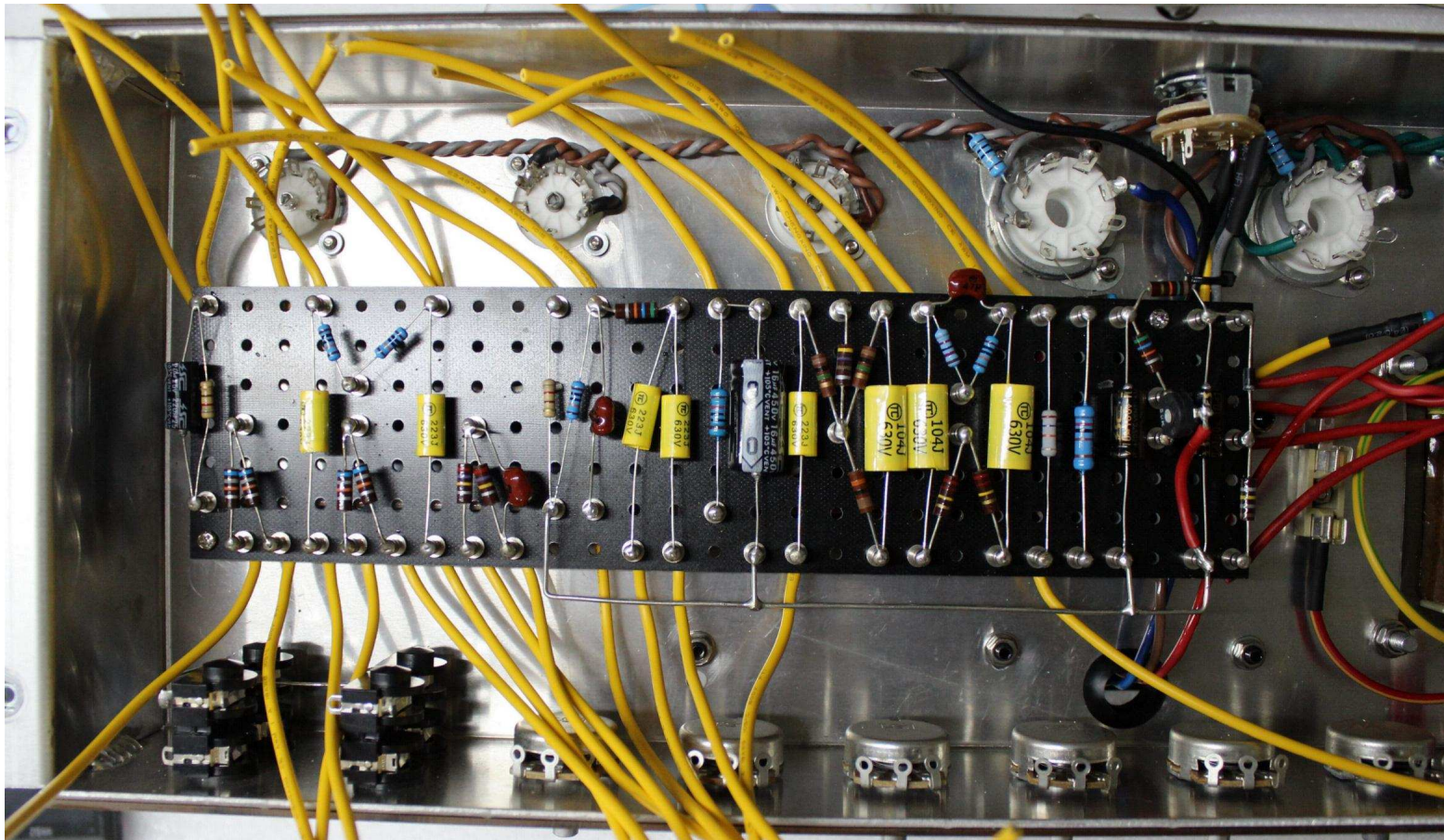10. Use a short red wire to connect the Center Pin of Main Fuse Holder to the "N" tab of AC Socket, see below pic:




11. Now load the PCB assembly into the chassis;






12. Tube 12AX7 No.1 wiring as follow:

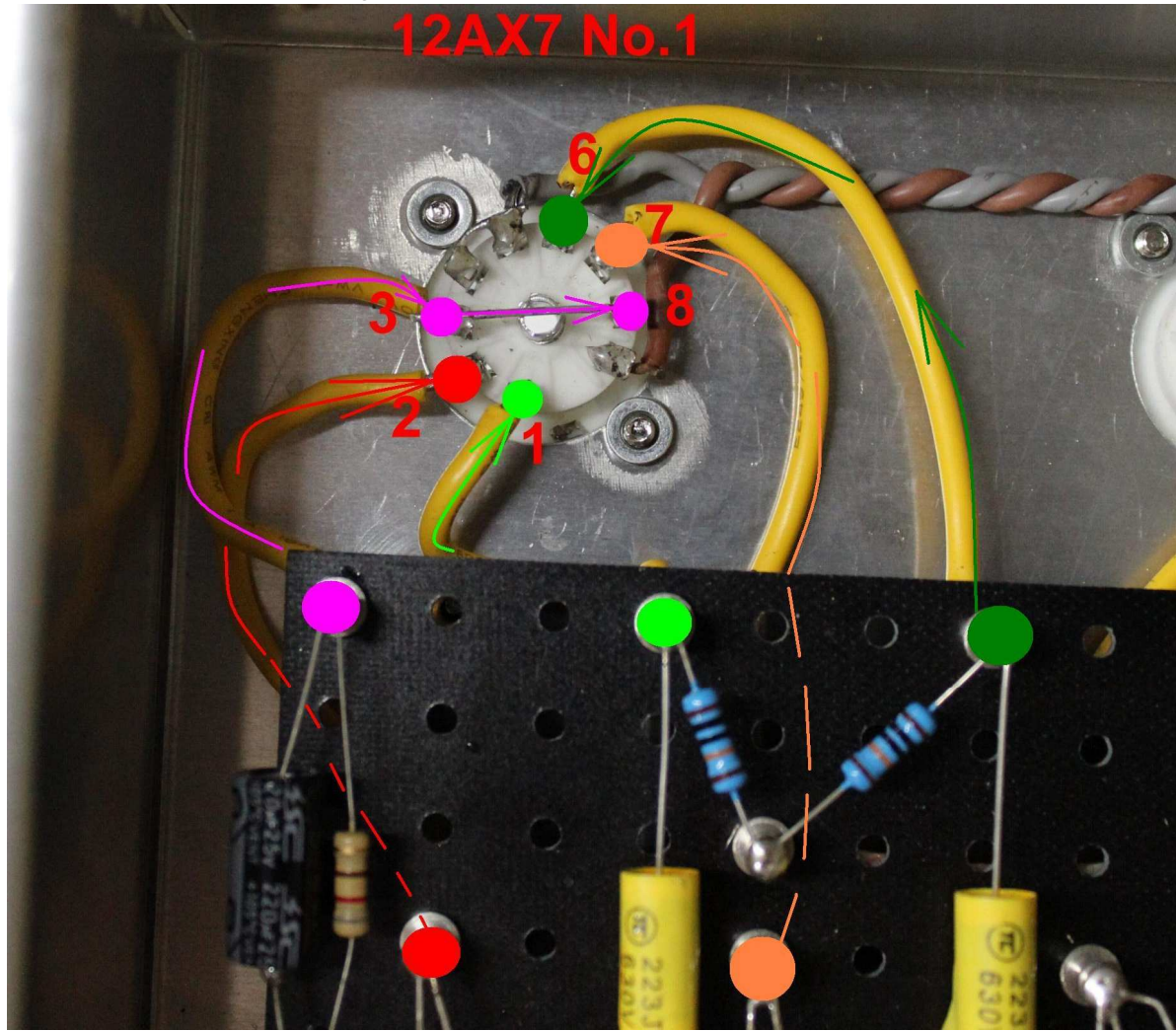


13. Tube 12AX7 No.2 wiring:

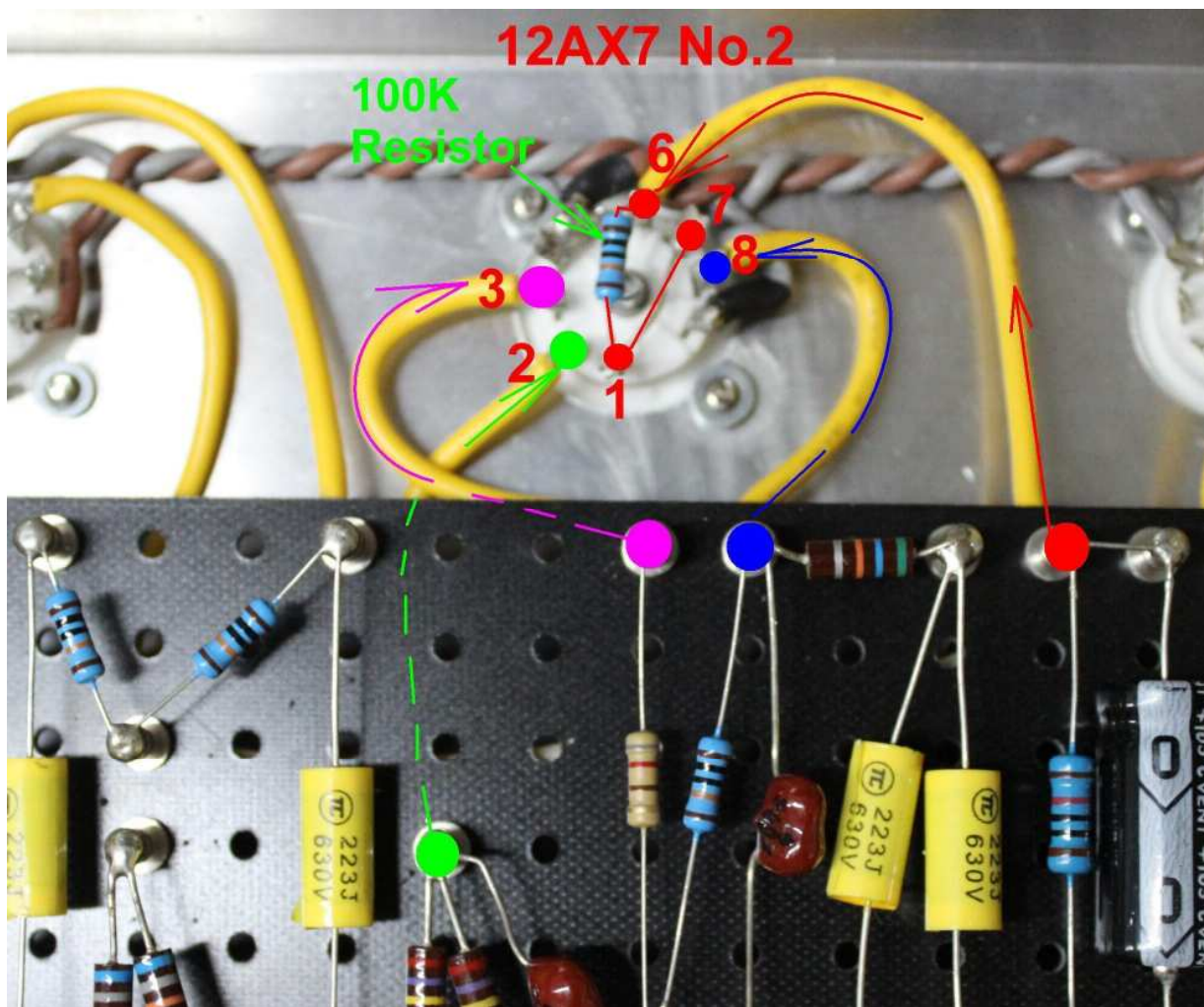



14. 12AX7 No.3 wiring:

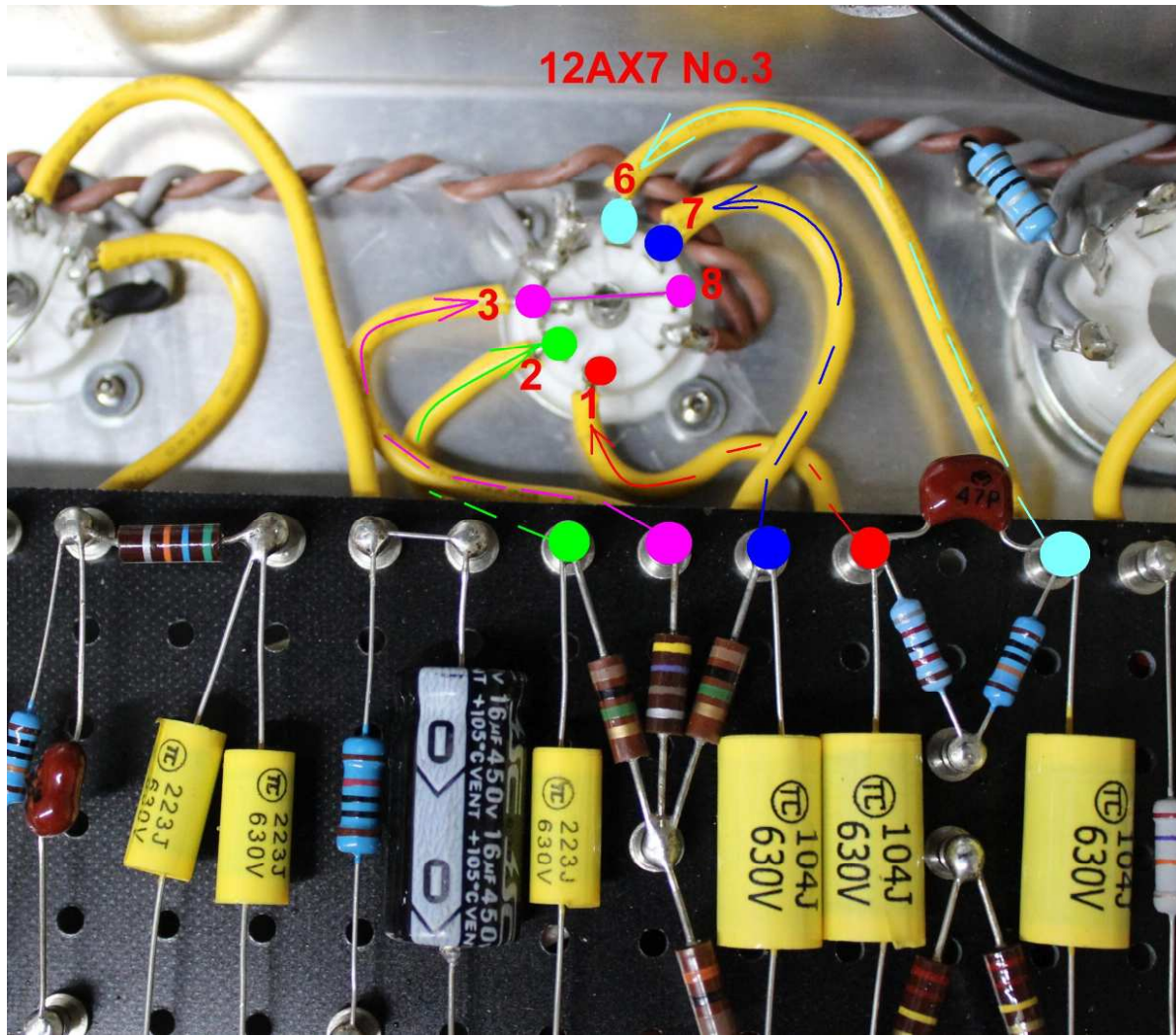

15. Output jack wiring1: use two solid jumper wires to connect both output jacks as follow:

